An active filter is a device for reducing harmonic distortion by supplying harmonic components

Classification : Parallel, Series, Unified

- Hybrid filters : Active + Passive
- Applications
- Modelling guidelines
- Example









SHUNT	SERIES		
Operates as a current source	Operates as a voltage source		
Voltage-fed PWM inverter with current minor loop	Voltage-fed PWM inverter without current minor loop		
Inductive, current-source loads, harmonic current sources	Capacitive, voltage-source loads, harmonic voltage sources		
High load impedance	Low load impedance		
Excellent and independent of the source impedance for current-source loads, but depend on the source impedance when the load impedance is low	Excellent and independent of the source and the load impedances for voltage-source loads, but depend on the source impedance for current-source type loads		
Reactive power compensation	Voltage regulation		
Commercial stage	Laboratory stage		
	SHUNT Operates as a current source Voltage-fed PWM inverter with current minor loop Inductive, current-source loads, harmonic current sources High load impedance Excellent and independent of the source impedance for current-source loads, but depend on the source impedance when the load impedance is low		



#### Scheme of the test system



#### **Detailed scheme of the power circuit**



#### **Control unit**



#### **PCC voltage and rectifier current**



#### **PCC voltage and source current**



**Rectifier and source currents** 



#### **PCC voltage and rectifier current**



#### **PCC voltage and source current**

### **Harmonic Distortion**

CASE	Current	RMS (A)	H1 (A)	THD (%)	H5 (%)	H7 (%)	H11 (%)	H13 (%)
1	Load	45.26	43.80	26.00	23.99	8.599	3.802	3.001
	Source	52.43	52.41	2.739	0.427	0.961	0.306	0.270
2	Load	67.43	49.39	92.96	73.70	52.90	16.43	8.357
	Source	59.15	59.02	6.374	3.707	4.089	0.903	1.776
3	Load	66.70	49.19	91.57	72.78	52.18	15.42	7.786
	Source	58.72	58.13	14.10	9.324	9.944	0.968	1.185





**Single-phase scheme** 



Voltage compensation
 Only magnitude
 Total compensation

$$U_{\text{comp}} = \sqrt{\left(U_{\text{p}} \cdot Cos \boldsymbol{q}_{\text{p}} - U_{\text{hdt}} \cdot Cos \boldsymbol{q}_{\text{hdt}}\right)^{2} + \left(U_{\text{p}} \cdot Sin \boldsymbol{q}_{\text{p}} - U_{\text{hdt}} \cdot Sin \boldsymbol{q}_{\text{hdt}}\right)^{2}}$$
$$= \sqrt{U_{\text{p}}^{2} + U_{\text{hdt}}^{2} - 2 \cdot U_{\text{p}} \cdot U_{\text{hdt}} \cdot Cos \boldsymbol{g}}; \qquad \boldsymbol{g} = \boldsymbol{q}_{\text{p}} - \boldsymbol{q}_{\text{hdt}}}$$

#### **'ab' transformation**

$$S_{ab} = S_{a} + j \cdot S_{b} = \sqrt{\frac{2}{3}} \cdot \left( S_{a} \cdot e^{j0} + S_{b} \cdot e^{j\frac{2\cdot p}{3}} + S_{c} \cdot e^{j\frac{4\cdot p}{3}} \right)$$

$$\begin{bmatrix} S_{a} \\ S_{b} \\ S_{0} \end{bmatrix} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \sqrt{3} & -\frac{\sqrt{3}}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \end{bmatrix} \cdot \begin{bmatrix} S_{a} \\ S_{b} \\ S_{c} \end{bmatrix}$$

$$\begin{bmatrix} S_{a} \\ S_{b} \\ S_{c} \end{bmatrix} = \sqrt{\frac{2}{3}} \cdot \begin{bmatrix} 1 & 0 & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & \frac{\sqrt{3}}{2} & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} & \frac{1}{\sqrt{2}} \end{bmatrix} \cdot \begin{bmatrix} S_{a} \\ S_{b} \\ S_{0} \end{bmatrix}$$

**'ab' transformation** 

$$v_{a}(t) = \mathbf{x} \cdot Cos(\mathbf{w}t + \mathbf{j}_{d}) + \mathbf{y} \cdot Cos(\mathbf{w}t + \mathbf{j}_{i})$$
$$v_{b}(t) = \mathbf{x} \cdot Cos(\mathbf{w}t + \mathbf{j}_{d} - \frac{2\mathbf{p}}{3}) + \mathbf{y} \cdot Cos(\mathbf{w}t + \mathbf{j}_{i} + \frac{2\mathbf{p}}{3})$$
$$v_{c}(t) = \mathbf{x} \cdot Cos(\mathbf{w}t + \mathbf{j}_{d} + \frac{2\mathbf{p}}{3}) + \mathbf{y} \cdot Cos(\mathbf{w}t + \mathbf{j}_{i} - \frac{2\mathbf{p}}{3})$$

$$\boldsymbol{a} = \sqrt{\frac{3}{2}} \cdot \left[ \mathbf{x} \cdot Cos(\boldsymbol{w}t + \boldsymbol{j}_d) + \mathbf{y} \cdot Cos(\boldsymbol{w}t + \boldsymbol{j}_i) \right] = \boldsymbol{a}_+ + \boldsymbol{a}_-$$
$$\boldsymbol{b} = \sqrt{\frac{3}{2}} \cdot \left[ \mathbf{x} \cdot Sen(\boldsymbol{w}t + \boldsymbol{j}_d) - \mathbf{y} \cdot Sen(\boldsymbol{w}t + \boldsymbol{j}_i) \right] = \boldsymbol{b}_+ + \boldsymbol{b}_-$$

**Symmetrical component calculation** 

$$\mathbf{a}_{+} = \frac{1}{2} \cdot \left[\mathbf{a} - \mathbf{b}_{(-p/2)}\right]$$
$$\mathbf{b}_{+} = \frac{1}{2} \cdot \left[\mathbf{a}_{(-p/2)} + \mathbf{b}\right]$$
$$\mathbf{a}_{-} = \frac{1}{2} \cdot \left[\mathbf{a} + \mathbf{b}_{(-p/2)}\right]$$
$$\mathbf{b}_{-} = \frac{1}{2} \cdot \left[\mathbf{a}_{(-p/2)} - \mathbf{b}\right]$$



# **Dynamic Voltage Restorer** Synchronous reference - 'dq' transformation

$$\begin{bmatrix} \mathbf{S}_d \\ \mathbf{S}_q \end{bmatrix} = \begin{bmatrix} Cos \mathbf{q} & Sen \mathbf{q} \\ -Sen \mathbf{q} & Cos \mathbf{q} \end{bmatrix} \cdot \begin{bmatrix} \mathbf{S}_a \\ \mathbf{S}_b \end{bmatrix}$$



#### **Calculation of the actual voltage compensation**

$$V_{\text{comp}} = \frac{1}{LC \cdot s^2 + RC \cdot s + 1} \cdot V_{\text{conv}} - \frac{R + L \cdot s}{LC \cdot s^2 + RC \cdot s + 1} \cdot (n \cdot I_{\text{load}})$$



#### **Control strategy**

- Measure system voltages and currents
- Apply 'ab' transform to voltages and currents, and obtain symmetrical components
- Obtain 'dq' components
- Determine voltage compensation in 'dq' values for positive and negative sequences
- Deduce the values to be obtained at the converter terminals, taking into account the passive filter effect
- Obtain compensation voltages by applying antitransforms ('dq' → 'ab' → 'abc')
- Determine gate signals by means of a PWM control strategy

#### **Test system**



#### Test cases

- Same voltage dip at the three phases
- Voltage dip in two phases, voltage swell in the third phase, with phase angle jumps



#### Input voltages



Load voltages



Voltages injected by the DVR



#### **Input voltages**



Load voltages



Voltages injected by the DVR



Phase - 'a'



Phase - 'b'



Phase - 'c'

### Stochastic Prediction of Voltage Dips

- The Monte Carlo method
- Diagram of the test system
- Assumptions
- Voltage dip calculations
  - voltage dip probability density
  - number of voltage dips
- Effect of protective devices

### **The Monte Carlo Method**

- A widely used technique for analyzing multidimensional complex systems
- It can be used for solving both stochastic and deterministic problems
- This technique is based on a iterative procedure that is repeated using in every new step a set of values of the random variables involved in the process, being these values generated according to the probability density function associated to each variable.

## Scheme of the Test System



HV equivalent : 110 kV, 1500 MVA, X/R = 10 Substation transformer : 110/25 kV, 10 MVA, 8%, Yd11 Distribution transformers: 25/0.4 kV, 1 MVA, 6%, Dy Lines :  $Z_{1/2} = 0.61 + j0.39$ ,  $Z_0 = 0.76 + j1.56$  Ω/km

### **Stochastic Prediction**

- Voltage dips are generated only by faults
- Characteristics of the faults
  - Fault location : It is selected by generating a uniform random number
  - Fault resistance: normal distribution, average value =10 S, standard deviation =1 S
  - Duration of the fault: normal distribution, average value = 0.06s, standard deviation =0.01 s
  - Initial time of the fault: uniform distribution between 0.04 and 0.06 s
  - Probability of each type of fault: LG: 80%, 2LG: 17%, 3LG: 0%, LL: 2%, 3L: 1%
- The test system was simulated 5000 times
- Assuming 12 faults per 100 km and year, this equals the performance of the network during 366 years



# Fault location probability density



# Fault resistance probability density



#### Initial fault time probability density



#### Fault duration probability density



#### Fault type probability



Dip density function at Node 4 - phase 'a' - after 1000 runs



Dip density function at Node 4 - phase 'a' - after 5000 runs

### **Protective devices**

Significant influence of protection devices Only reclosers have been simulated Very simple model based on a delay and a reclosing interval Only one reclosing operation Dip density function considering different reclosing intervals : 100 and 120 ms • Number of dips per year and phase, with and without reclosers

### **Protective devices**



#### A (with Recloser) A (without Recloser) RMS Voltage (kV) Time (ms)

# Voltage at a node located in the faulted feeder

# Voltage at a node located in the unfaulted feeder



Dip density function at Node 4 - phase 'a' Reclosing interval : 100 ms



Number of dips per year at Node 4 - phase 'a' Without recloser



Number of dips per year at Node 4 - phase 'a' With recloser - Reclosing interval : 100 ms

### Conclusions

- EMTP-like tools are sophisticated packages that are regularly updated and expanded
- They tools provide capabilities for obtaining transient and harmonic solutions, and representing nonlinear and frequency-dependent components
- They are very efficient to predict disturbance effects and to evaluate new mitigation techniques, but their capabilities are very limited to represent semiconductors
- There is a growing trend towards open systems, with the design of more efficient interfaces and the improvement of postprocessing capabilities